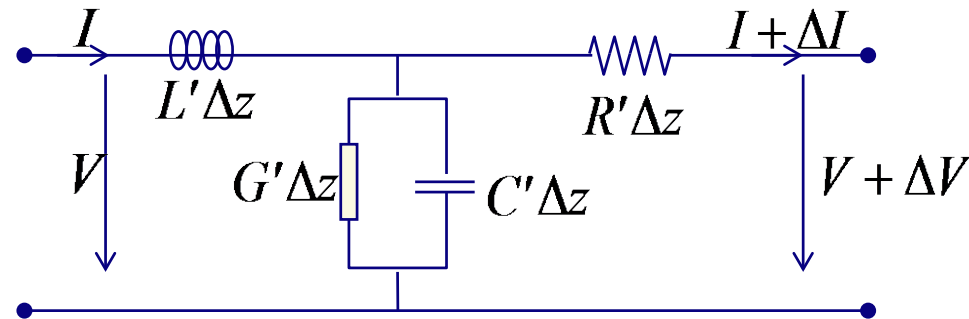


ECE 222b
Applied Electromagnetics
SET 2

Instructor: Dr. Vitaliy Lomakin
Department of Electrical and Computer Engineering
University of California, San Diego, IL 61801-2991

Review of Transmission Line (1)

Consider a segment of a transmission line:



Kirchhoff's laws:

$$V = j\omega L\Delta z I + R\Delta z(I + \Delta I) + V + \Delta V$$



$$\frac{dV}{dz} + (j\omega L + R)I = 0$$

$$I = G\Delta z V + j\omega C\Delta z V + I + \Delta I$$



$$\frac{dI}{dz} + (j\omega C + G)V = 0$$

Review of Transmission Line (2)

Try to eliminate I :
$$\frac{d^2V}{dz^2} + (j\omega L + R)\frac{dI}{dz} = 0$$

$$\frac{d^2V}{dz^2} - (j\omega L + R)(j\omega C + G)V = 0$$

$$\frac{d^2V}{dz^2} - \gamma^2 V = 0$$

$$\gamma^2 = (j\omega L + R)(j\omega C + G)$$



Propagation constant

Similarly,

$$\frac{d^2I}{dz^2} - \gamma^2 I = 0$$

Review of Transmission Line (3)

Consider a lossless line:

$$R = 0, \quad G = 0 \quad \Rightarrow \quad \gamma = j\omega\sqrt{LC} \quad \begin{array}{l} \text{Phase} \\ \text{constant} \end{array}$$

$$\gamma = j\beta \quad \beta = \omega\sqrt{LC}$$

$$\frac{d^2V}{dz^2} + \beta^2V = 0 \quad \Rightarrow \quad V(z) = a_+e^{-j\beta z} + a_-e^{j\beta z}$$

Consider $V_+(z) = a_+e^{-j\beta z}$ Wave traveling toward +z direction!

$$V_+(z, t) = \text{Re}[V_+(z)e^{-j\omega t}] = \text{Re}(a_+e^{j\omega t - j\beta z})$$

$$= |a_+| \cos(\omega t - \beta z + \angle a_+)$$

$$\omega t - \beta z_p = \text{constant} \quad \Rightarrow \quad \omega - \beta \frac{dz_p}{dt} = 0 \quad \Rightarrow \quad \frac{dz_p}{dt} = \frac{\omega}{\beta}$$

Phase velocity

Review of Transmission Line (4)

Consider a lossy line:

$$\gamma = \sqrt{(j\omega L + R)(j\omega C + G)} = \alpha + j\beta$$

$$\frac{d^2V}{dz^2} - \gamma^2 V = 0 \quad \longrightarrow \quad V(z) = a_+ e^{-\gamma z} + a_- e^{\gamma z}$$

Consider $V_+(z) = a_+ e^{-\gamma z} = a_+ e^{-(\alpha + j\beta)z}$

$$\begin{aligned} V_+(z, t) &= \operatorname{Re}\left[V_+(z) e^{j\omega t}\right] = \operatorname{Re}\left(a_+ e^{j\omega t - j\beta z - \alpha z}\right) \\ &= |a_+| e^{-\alpha z} \cos(\omega t - \beta z + \angle a_+) \end{aligned}$$

α : attenuation constant β : phase constant

Review of Transmission Line (5)

Consider the general case:

$$V(z) = a_+ e^{-\gamma z} + a_- e^{\gamma z}$$

Define

$$\Gamma = \frac{V_-(0)}{V_+(0)} = \frac{a_-}{a_+} \Rightarrow V(z) = a_+ e^{-\gamma z} + a_+ \Gamma e^{\gamma z}$$

Reflection coefficient:

$$\Gamma(z) = \frac{V_-(z)}{V_+(z)} = \frac{a_- e^{\gamma z}}{a_+ e^{-\gamma z}} = \Gamma e^{2\gamma z}$$

$$\begin{aligned} \Gamma(z_1) &= \Gamma e^{2\gamma z_1} \\ \Gamma(z_2) &= \Gamma e^{2\gamma z_2} \end{aligned} \Rightarrow \Gamma(z_1) = \Gamma(z_2) e^{2\gamma(z_1 - z_2)}$$

Review of Transmission Line (6)

Find the current:

$$\frac{dV}{dz} = -\gamma a_+ e^{-\gamma z} + \gamma a_+ \Gamma e^{-\gamma z} = -(j\omega L + R)I$$

$$\begin{aligned} I(z) &= \frac{\gamma}{j\omega L + R} a_+ e^{-\gamma z} - \frac{\gamma}{j\omega L + R} a_+ \Gamma e^{\gamma z} \\ &= \frac{\gamma}{j\omega L + R} a_+ (e^{-\gamma z} - \Gamma e^{\gamma z}) \end{aligned}$$

Define the **characteristic impedance**:

$$Z_0 = \frac{V_+}{I_+} = \frac{j\omega L + R}{\gamma} = \sqrt{\frac{j\omega L + R}{j\omega C + G}}$$

Review of Transmission Line (7)

Impedance at z :

$$Z(z) = \frac{V(z)}{I(z)} = \frac{a_+ e^{-\gamma z} + a_+ \Gamma e^{\gamma z}}{\frac{1}{Z_0} a_+ (e^{-\gamma z} - \Gamma e^{\gamma z})} = Z_0 \frac{1 + \Gamma e^{2\gamma z}}{1 - \Gamma e^{2\gamma z}} = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

$$Z(z) = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

$$\Gamma(z) = \frac{Z(z) - Z_0}{Z(z) + Z_0}$$


- Observation:**
1. Z_0 is independent of z
 2. $Z(z)$ depends on z
 3. $\Gamma(z)$ depends on z
 4. For a lossless line, $\gamma = j\beta$

$$|\Gamma(z)| = |\Gamma e^{2j\beta z}| = |\Gamma| \text{ is invariant along } z$$

Review of Transmission Line (8)

Typical problem:

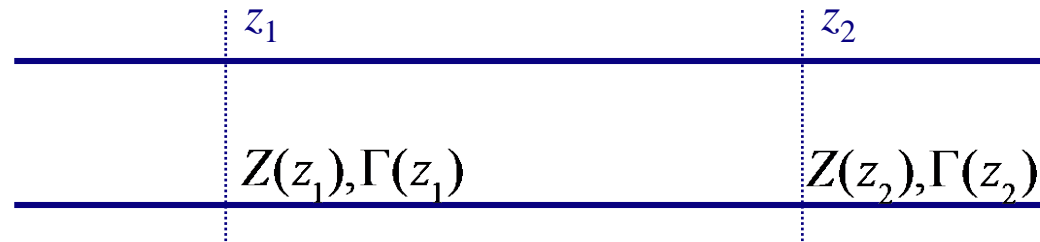Given information at z_1 , find information at z_2



$$\Gamma(z) = \Gamma e^{2\gamma z} \quad \Rightarrow \quad \Gamma(z_2) = \Gamma(z_1) e^{2\gamma(z_2 - z_1)}$$

$$Z(z_2) = Z_0 \frac{1 + \Gamma(z_2)}{1 - \Gamma(z_2)} = Z_0 \frac{1 + \Gamma(z_1) e^{2\gamma(z_2 - z_1)}}{1 - \Gamma(z_1) e^{2\gamma(z_2 - z_1)}}$$

$$Z(z_1) = Z_0 \frac{1 + \Gamma(z_1)}{1 - \Gamma(z_1)} \quad \Rightarrow \quad \Gamma(z_1) = \frac{Z(z_1) - Z_0}{Z(z_1) + Z_0}$$

Review of Transmission Line (9)

$$Z(z_2) = Z_0 \frac{1 + \frac{Z(z_1) - Z_0}{Z(z_1) + Z_0} e^{2\gamma(z_2 - z_1)}}{1 - \frac{Z(z_1) - Z_0}{Z(z_1) + Z_0} e^{2\gamma(z_2 - z_1)}} = Z_0 \frac{Z_1 + Z_0 + (Z_1 - Z_0)e^{2\gamma(z_2 - z_1)}}{Z_1 + Z_0 - (Z_1 - Z_0)e^{2\gamma(z_2 - z_1)}}$$

$$Z(z_2) = Z_0 \frac{Z_1(e^{\gamma l} + e^{-\gamma l}) - Z_0(e^{\gamma l} - e^{-\gamma l})}{Z_1(e^{-\gamma l} - e^{\gamma l}) + Z_0(e^{\gamma l} + e^{-\gamma l})} \quad l = z_2 - z_1$$

$$= Z_0 \frac{Z_1 \cosh \gamma l - Z_0 \sinh \gamma l}{Z_0 \cosh \gamma l - Z_1 \sinh \gamma l}$$


For a lossless line: $\gamma = j\beta$

$$Z_2 = Z_0 \frac{Z_1 \cos \beta l - jZ_0 \sin \beta l}{Z_0 \cos \beta l - jZ_1 \sin \beta l}$$

$$Z_1 = Z_0 \frac{Z_2 \cos \beta l + jZ_0 \sin \beta l}{Z_0 \cos \beta l + jZ_2 \sin \beta l}$$

Review of Transmission Line (10)
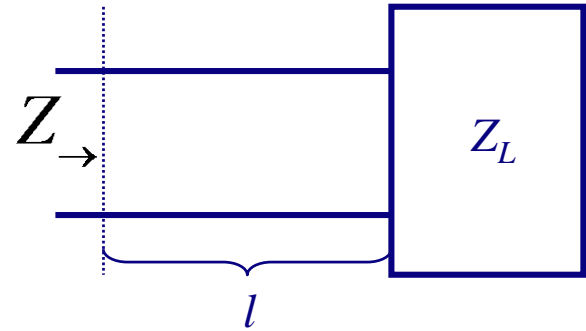
$$Z_{\rightarrow} = Z_0 \frac{Z_L \cos \beta l + jZ_0 \sin \beta l}{Z_0 \cos \beta l + jZ_L \sin \beta l}$$



If $Z_L = 0$, $Z_{\rightarrow} = jZ_0 \tan \beta l$

If $Z_L = \infty$, $Z_{\rightarrow} = -jZ_0 \cot \beta l$

Z_{\rightarrow} = input impedance